

RGPV BASED ASSIGNMENT QUESTION.

SUBJECT- CNTL (EC-505)

BRANCH- EC 5TH SEM

INSTRUCTIONS. 1. All questions with their solution are submitted till 27 October 2014.

Q 1 Design an asymmetrical T-attenuator to produce attenuation of 20 db and to work between source impedance of 200 ohm and load impedance of 800 ohm.

Q 2 Design a m-derive t-section low pass filter having cut off frequency $f_c=1000\text{Hz}$, design impedance $R_k=600 \Omega$ and frequency of infinite attenuation $f_\infty=1050 \text{ Hz}$.

Q 3 Find the network for the impedance function using foster-1 form:

$$Z(s) = \frac{(s+1)(s+3)}{S(s+2)}$$

Q 4 Find the network in each case using the given method:

$$(1) Z(s) = \frac{2s^2+s+1}{S^3+s^2+s+1} \quad [\text{using foster 1 form}]$$

$$(2) Z(s) = \frac{6+8s^2+2s^4}{2s+s^3} \quad [\text{using Cauer-2 form}]$$

Q 5 Calculate the iterative and image impedance of a T- network with series and shunt impedance arm impedance Z_1 and Z_2 and Z_3 , $Z_1 = 30+j7.5 \Omega$, $Z_2 = 50+j10 \Omega$, and $Z_3 = -j3.229 \Omega$.

Q 6 What do you mean by SWR? A loss line with $Z_o=70 \Omega$ is terminated in an impedance $Z_r = 115-j80 \Omega$.

The wavelength of the transmission is 2.5 m using the given smith chart find the following :

- Standing wave ratio
- Maximum and minimum line impedance.
- Distance between the load and first voltage maxima.

Q 7 A transmission line has a characteristic impedance of 600Ω . determine the magnitude of the reflection coefficient if the receiving end impedance is $650-j475 \Omega$

Q 8 Design constant- K bandstop filters(both T and π section) for the cut off frequency of 2 khz and 6 khz . the impedance is 500Ω

Q 9 Design an m-derive low pass filter with a cut off frequency of 2 khz . design impedance 500 and $m=0.4$ consider a π section for your coluction.

Q 10 The constant of a Transmission Line are $R=6\Omega/\text{km}$, $L =202\text{Mh}/\text{km}$, $C=0.005\mu\text{F}/\text{Km}$ and $G=0.25*10^{-3}\text{mhos}/\text{km}$. calculate the attenuation constant and phase constant at 1000Hz

Q 11 A single stub is to match a 300Ω line to a load of $(180+j120) \Omega$ the wavelength is 2m . Determine the shortest distance from the load to the stub location and proper length of the short circuited stub using relevant formula.

Q 12 The driving point impedance of an LC network is given by

$$Z(s) = \frac{10s^3 + 4s}{15s^4 + 10s^2 + 1}$$

Q 13 At a point on a transmission line the line impedance is $(75+j75)\Omega$ and the characteristic impedance of line is 75Ω . Use a smith chart to find the line admittance at a point. Check the answer by direct calculation

Q 14 Design a band elimination filter having a design impedance of 500Ω and cut-off frequency 1kHz and 10kHz .